

EENG-331 Lab 5:

CS stage Design and Audio Processing

1 Prelab

1.1 Common Source Amplifier With Resistor Biasing and Passive Load

Prior to the lab, each team member designed a Common Source Stage with resistor divider biasing and resistor load, for $A_v = 10$, $5mW$ power budget, $V_{ov} = 100mV$, $k_p = \frac{100\mu A}{V^2}$, $V_{dd} = 5V$, $\lambda = 0$, and $V_{th} = 0.5V$. Additionally, it was assumed that an "investment" of 10% of the power budget on setting the gate voltage was intended. Finally, we assumed that $L = 10\mu m$ is the smallest allowable value for the design. The hand-calculations for this amplifier design can be seen in Figure(1). The resulting design has values as follows:

$$P_{\text{power consumed by } I_d} = 90\% \cdot 5mW = 4.5mW \quad (1)$$

$$I_d = \frac{4.5mW}{5v} = 0.9mA \quad (2)$$

$$I_d = 0.9mA = \frac{1}{2}k_p \frac{W}{L} V_{ov}^2 \rightarrow \frac{W}{L} = \frac{18000\mu}{10\mu} = 1800 \quad (3)$$

$$g_m = \frac{2I_d}{V_{ov}} = 18mS \quad (4)$$

$$A_v = -g_m R_d \rightarrow |A_v| = g_m R_d \rightarrow R_d = 556\Omega \quad (5)$$

$$V_{g,dc} = V_{th} + V_{ov} = 0.6v \quad (6)$$

$$I_{\text{gate voltage divider}} = \frac{10\% \cdot 5mW}{5v} = 0.1mA \quad (7)$$

$$R_2 = \frac{0.6V}{0.1mA} = 6k\Omega \quad (8)$$

$$R_1 = \frac{5V - 0.6V}{0.1mA} = 44k\Omega \quad (9)$$

1.2 Common Source Amplifier With Self-Biasing, Active Load

Additionally, a CS stage was designed using a current source for the load, and the self-biasing method for setting the gate voltage. This stage follows all the same constraints as the previous section.

Regarding I_d , the instructions say to use the same I_d as the previous stage. This would be only $0.9mA$, and also did not seem to be in alignment with email communications received about the lab calculations. We instead chose to interpret this as "Use the same power budget", which results in $I_d = 1mA$, and is consistent with the other communications received.

Before presenting the calculations, know that an oversight was made on the gain of the stage initially, but quickly corrected after the start time of the lab. Since the prelab was due at the start of the lab, we

present the initial flawed calculations in the scan of the prelab, but the correct calculations in this lab report. The flawed calculations can be seen in Figure(2).

The mistake made was to take the gain equation for CS w/ active load, $A_v = g_m r_o$, and use it with $\lambda = 0$, but mistakenly behave as if $r_o \neq \infty$ in that case, which gave $A_v = \overline{g_m}$, suggesting a need for a very large g_m . It is believed that a contributing factor to the mistake was the nonsensical correct result: $r_o = \infty$, which is fine, but $A_v = g_m \cdot \infty = \infty$, which would make it impossible to meet the $A_v = 10$ constraint.

The calculations for this stage are much more simple. Self-biasing will set V_g . We simply need to choose $\frac{W}{L}$ such that $V_{ov} = 0.1$, to match the constraint. We take Equation(3), and recalculate $\frac{W}{L}$ for $I_d = 1mA$, returning Equation(10).

$$I_d = 1mA = \frac{1}{2}k_p \frac{W}{L} V_{ov}^2 \rightarrow \frac{W}{L} = \frac{20000\mu}{10\mu} = 2000 \quad (10)$$

The choice of R_g is arbitrary, but it is worth noting that R_g results in coupling between V_{in} and V_{out} . Since a CS stage is an inverting amplifier, this makes the coupling a negative feedback to the input, degrading our overall gain. In our simulations we are using a voltage source with no series resistance for V_{in} ; as a result this effect is not seen except as an interaction with the input coupling capacitor, which we can suppress by making the capacitor arbitrarily large.


1/

EEENG-331 Prelab 5 Jeremy Munson

a. Watch the Lab Video \rightarrow Done
 $\frac{W}{L} = \frac{36000}{10}$ (From video)

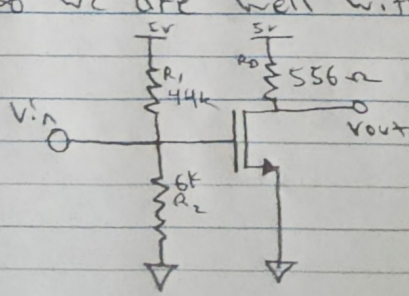b. Design a CS Stage without source degeneration
 $A_v = 10$, Power = 5mW, $\lambda = 0$, $V_{ov} = 100mV$
 $K_p = 100 \frac{\mu A}{V^2}$, $V_{DD} = 5V$, $V_{th} = 0.5V$
 I don't know what portion you want invested in gate voltage divider, so using W/L from video.

- $I_D = \frac{1}{2} K_p V_{ov}^2 \cdot \frac{W}{L} = \frac{1}{2} \frac{100 \mu A}{V^2} 3600 (0.01V^2)$
 $= 1.8mA \rightarrow P = 9mW$... VMM... That will not work.
- Backing up, let's invest 10% \rightarrow
 $I_D \cdot 5V = 4.5mW \rightarrow I_D = .9mA$
 $.9mA = \frac{1}{2} \frac{100 \mu A}{V^2} .01V^2 \cdot \frac{W}{L} \rightarrow W/L = 1800 \rightarrow L=10 \quad W=18000$
- $g_m = \frac{2I_D}{V_{ov}} = \frac{1.8mA}{.1V} = 18mS$
- $A_v = -g_m R_D \rightarrow 10 = -.018 R_D \rightarrow R_D = 556 \Omega$
- Now for R_1, R_2
 $V_{ov} = .1V$, $V_{th} = .5V$, $\therefore V_G = .6V$
 There is .1mA "left over" from before, so
 $.6V = .1mA R_2 \rightarrow R_2 = 6K$, $R_1 = 44K$
- Check that we are in Sat.
 $I_D \cdot R_D = .0009 \cdot 556 = 0.5V$
 Then by KVL, $V_{GS} = 4.5V \rightarrow 4.5 > 0.1$
 So we are well within Saturation




just in case, IF gate bias current neglected, then $I_D = 1mA$
 and $A_v = g_m R_D$
 $g_m = \frac{2I_D}{V_{ov}}$
 $\rightarrow R_D = 500 \Omega$

Figure 1: Prelab Calculations for CS amplifier with resistor load & biasing

2/

 - FENG 331 Ptlab 5 Jeremy Munson
- c. Design Cs with same constraints, but self-biasing (use same I_D)
- Using the same I_D would not consume the full power budget, was it meant that we draw the same total current?



$$g_m = \sqrt{2 k_p \frac{W}{L} I_D} \rightarrow 100 = 2 \cdot \frac{100 \mu A}{V_t} \cdot 1 mA \cdot \frac{W}{L}$$

$$\frac{W}{L} = 5,000,000,000 \text{ which is a Lot}$$

If $\lambda \neq 0$, Then $A_v = -g_m r_o$, and $\frac{W}{L}$ would be much more reasonable

Also, just in case, with $I_D = 0.9 mA$
 $\frac{W}{L} = 5.5 \times 10^9$

Figure 2: Mistaken Prelab Calculations for CS amplifier w/ active load and self-biasing

2 Task 1

2.1 Parts a,b: Plot and Attenuate Harvey Super Cool, Save output to file

2.1.1 Tasks

- Import a .wav file into LTSpice and use it as a voltage source.
- Attenuate the signal by a factor of $\frac{1}{201}$ using a voltage divider.
- Plot the waveform before and after attenuation.
- Save the resulting attenuated waveform to a file.

2.1.2 Calculations

In order to attenuate the signal with a voltage divider, we must calculate the values of the resistors in the divider. Only the ratio matters for this, not the magnitudes. For this reason, the convenient value of $R_2 = 1\Omega$ is chosen. This is shown in Equation(11).

$$\frac{1}{201} = \frac{R_2}{R_1 + R_2} \rightarrow R_1 = 200\Omega, R_2 = 1\Omega \quad (11)$$

2.1.3 Description, Observation

We prepared the LTSpice schematic according to the lab instructions and prelab video, as can be seen in Figure(3). Here V_1 is a voltage source using the input .wav file, R_1 and R_2 form the voltage divider for attenuation, wav_attenuated is the name of the net at the output of the voltage divider, and we add in an additional spice directive, .wave, which instructs LTSpice to save the specified raw data as a .wav file with a particular name, bit depth, and sample rate.

We ran the simulation with the transient analysis settings specified in the lab document, and plot the input and attenuated output, resulting in the plots of Figure(4). It can be seen that the maximum voltage swing on the input waveform is $\pm 1V$ while the output waveform appears to be $\pm 5mV$. Measurement of the waveform in LTSpice (not shown) shows the attenuated waveform has an actual full-scale voltage of $\approx \pm 4.975mV$.

After running the transient analysis, a file is created from the attenuated output. We played this file using an audio player, as can be seen in Figure(5). The resulting audio was very quiet, and we had to turn the computer audio up to "150%" to hear it. Turning the volume up this high did not cause any audio clipping or artifacts that were observed.

2.1.4 Analysis

The voltage divider worked exactly as expected, as seen in Figure(4). The associated waveform measurements confirmed our attenuation by a factor of $\frac{1}{201}$. Playing the audio file that was exported also confirmed that the audio was successfully attenuated. We can also see that, since there was no observed clipping or distortion in the sound played afterwards when the computer volume was turned up past 100%, that the signal is indeed attenuated.

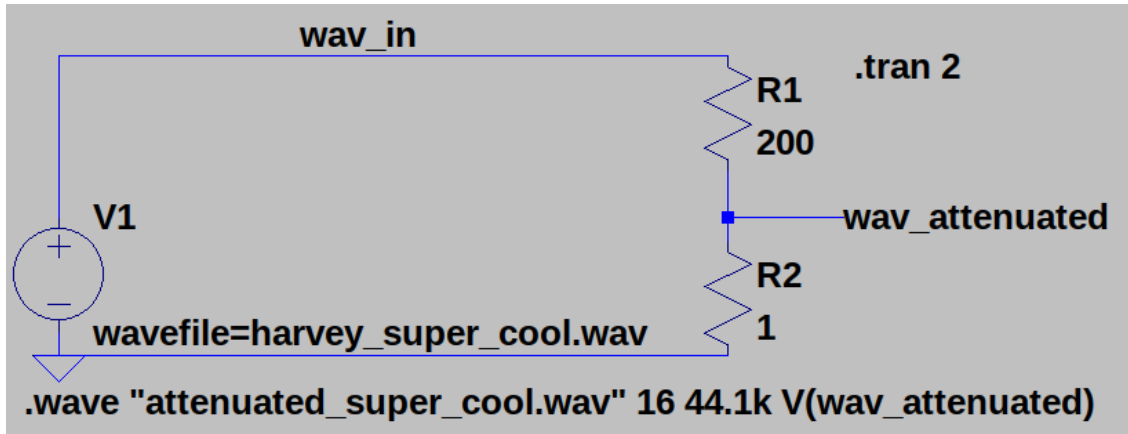


Figure 3: LTSpice schematic for a the .wav file import, voltage divider attenuation, and export

2.2 Part c: CS Stage Schematic

2.2.1 Tasks

- Use the values from prelab part (b) to create an LTSpice schematic for the CS Stage

2.2.2 Description

The schematic was created using the values from Figure(1), and an arbitrary choice of capacitance of $100\mu F$ for the input and output capacitors. The resulting schematic can be seen in Figure(6).

Then LTSpice tries to find an initial operating point value at the output capacitor for purposes of running the transient analysis, there is a short period where the output voltage would not be centered around $0V$. The addition of a $1M\omega$ resistor on the output suppresses this effect.

2.3 Part d: CS Stage Operating Point

2.3.1 Tasks

- Run a .op analysis and verify the operating point matches our expectations from the prelab

2.3.2 Description

We ran the .op analysis, the results of which are in Figure(7). The key values to compare with the prelab in Figure(1) are as follows:

- $V_g = 0.6V$ Matches the .op value of $V_{(n003)} = 0.6V$
- $I_d = 900\mu A$ Matches the .op value of $I_{d(M1)} = 0.0009V$
- Gate bias current of $100\mu A$ matches .op value of $I_{(R1)} = 0.0001V$
- Total Current of $1mA$ matches .op value of $I_{(V2)} = -.001A$

Additionally, the spice error log (not shown) shows $g_m = 1.8e-02$, $V_{gs} = 6.00e-01$, and $V_{ds} = 4.5e+00$. These values are all exactly what is expected from the prelab calculations.

 


Figure 4: Plots comparing the input Harvey Super Cool audio, and the attenuated output waveform.

2.4 Parts e, f: CS Stage .tran Test w/ 1mv sin and audio

2.4.1 Tasks

- Run a .tran simulation and verify the operation of the amplifier with a 1mv sine wave at 100hz
- Run a .tran simulation using the attenuated audio file as input and verify the circuit operation.

2.4.2 Description

The 1mv input was fed into the device in a transient analysis, and the waveforms compared in Figure(8). A gain of $|A_V| = 10$ is observed, with an amplitude reversal because this is an inverting amplifier. This matches our calculated values for gain in the prelab when we include the amplitude reversal for an inverting amplifier.

The amplitude reversal could be seen as a 180 deg phase shift for the pure, periodic sine wave, but phase shifting implies time-shifting as well. If a signal containing multiple components or that was aperiodic were to be fed into a black box with "180 degree phase shift" on the sticker, then the result would be

 


Figure 5: Playing the attenuated output audio

different than simple amplitude reversal. For this reason we prefer not to characterize this as a "phase shifting" action.

Next, we changed the input over to the attenuated audio file from the previous parts of this task. The resulting waveforms can be seen in Figure(9). The audio is re-amplified from $\approx \pm 5mV$ to $\approx \pm 50mv$, demonstrating that the amplifier worked exactly as expected. It is also worth noting that the amplitude has in fact been reversed between the input and output; this can be observed by looking closely at the peaks in the figure, as the waveform is not symmetrical about 0v.

Overall, the amplifier performed exactly as expected.

2.5 Part g: Increasing input impedance

- Increase the input impedance of the design to $100k\Omega$
- Verify that the design still works.

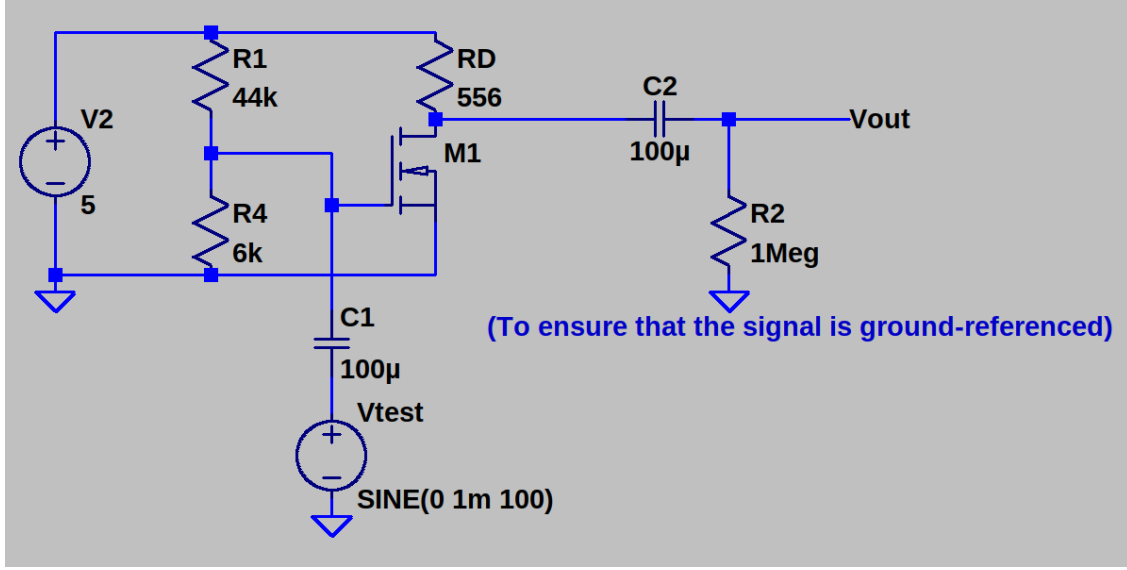


Figure 6: CS Stage W/Resistor Bias and Load, Schematic

2.6 Calculations

The increase the input impedance, we can increase the values of the resistors forming the biasing resistor divider. The current input impedance is given by Equation(12):

$$R_{in} = (R_1^{-1} + R_2^{-1})^{-1} = (44000\Omega^{-1} + 6000\Omega^{-1})^{-1} = 5280\Omega \quad (12)$$

If we don't bother to change the rest of the amplifier circuit design, then we will come in at a lower current, and lower overall power consumption. The difference is minor, so we simply adjust the voltage divider here.

The easiest way to increase the impedance will be to scale the voltage divider: Increase each resistor by a fixed factor. To do this, we write the ratio in Equation(13):

$$\frac{R_{in_{after}}}{R_{in_{before}}} = \frac{100000}{5280} \rightarrow R_{after} = R_{before} \cdot \frac{10000}{528} \quad (13)$$

Which results in $R_1 = 833333\Omega$ and $R_2 = 113636\Omega$.

We make those value changes, and plot the resulting waveform in Figure(10). It can be seen that the amplifier still has a gain of $A_v = -10$ and functions exactly the same as before.

2.7 Part h: Can the gain be increased to 200?

We are asked if the gain of the amplifier could be increased to 200. The answer is "Yes, but". First, we address the "yes".

The gain of the amplifier is used to calculate R_D in Equation(5). The gain is the product of R_D and g_m . Our g_m is fixed if we keep the same power budget, but we can increase R_D without limit. For this reason, we can make the gain arbitrarily large, including a value of 200.

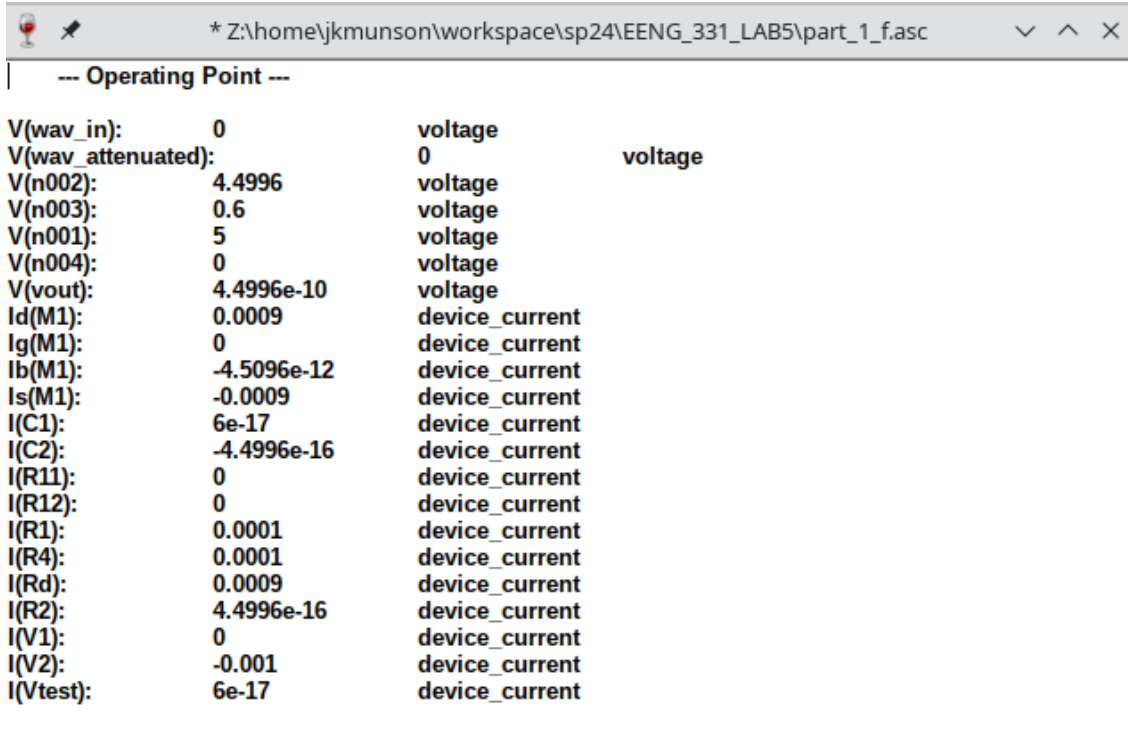


Figure 7: CS Stage W/Resistor Bias and Load, Operating Point Analysis

 


Figure 8: CS Stage W/Resistor Bias and Load, test with 1mv input

Now, for the "no": The gain is limited by the channel modulation effects in a real mos device. The gain for a real mos device would be given by Equation(14):

$$A_v = g_m \cdot (R_D \parallel r_o) \quad (14)$$

So we see that as we increase R_D , eventually we get Equation(15):

$$\lim_{R_D \rightarrow \infty} \dots, \quad A_V = g_m \cdot r_o \quad (15)$$

So the overall gain would be limited by the value of r_o , which is proportional to λ . For $\lambda \neq 0$, we may or may not be able to reach a gain of 200. In other words, with real mos devices we are limited to the intrinsic gain of the device.

From a different angle, If the gain were 200 then we would clip our audio signal. Since $V_{ds,dc} = 4.5V$, we have significantly less headroom than would be needed for the $\pm 1V$ output.

 


Figure 9: CS Stage W/Resistor Bias and Load, re-amplify the audio

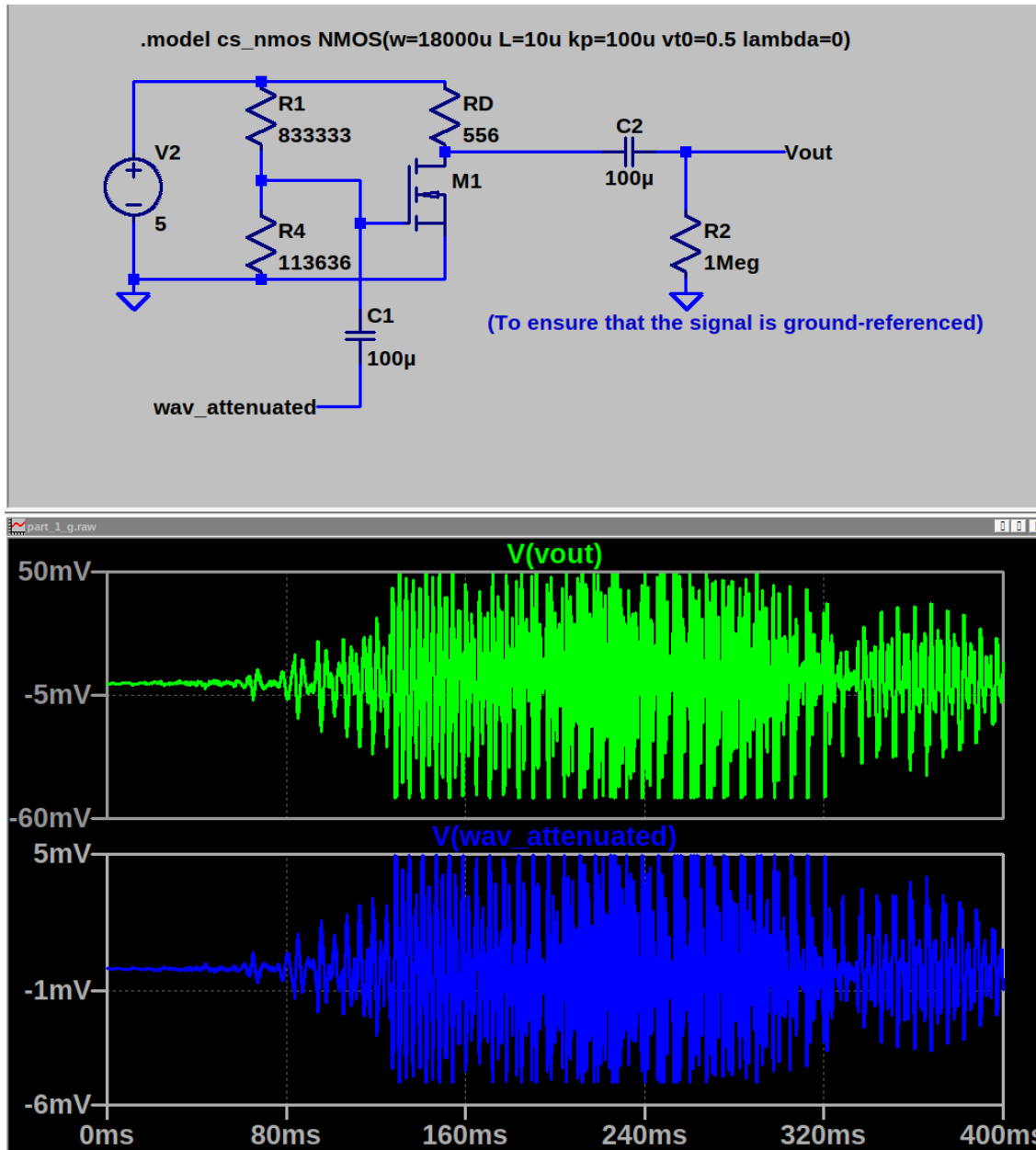


Figure 10: CS Stage W/input impedance increased.

Contents

1 Prelab	1
1.1 Common Source Amplifier With Resistor Biasing and Passive Load	1
1.2 Common Source Amplifier With Self-Biasing, Active Load	1
2 Task 1	5
2.1 Parts a,b: Plot and Attenuate Harvey Super Cool, Save output to file	5
2.2 Part c: CS Stage Schematic	6
2.3 Part d: CS Stage Operating Point	6
2.4 Parts e, f: CS Stage .tran Test w/ 1mv sin and audio	7
2.5 Part g: Increasing input impedance	8
2.6 Calculations	9
2.7 Part h: Can the gain be increased to 200?	9

Table Of Contents	13
--------------------------	-----------

List of Figures

1 Prelab Calculations for CS amplifier with resistor load & biasing	3
2 Mistaken Prelab Calculations for CS amplifier w/ active load and self-biasing	4
3 LTSpice schematic for a the .wav file import, voltage divider attenuation, and export . . .	6
4 Plots comparing the input Harvey Super Cool audio, and the attenuated output waveform.	7
5 Playing the attenuated output audio	8
6 CS Stage W/Resistor Bias and Load, Schematic	9
7 CS Stage W/Resistor Bias and Load, Operating Point Analysis	10
8 CS Stage W/Resistor Bias and Load, test with 1mv input	10
9 CS Stage W/Resistor Bias and Load, re-amplify the audio	11
10 CS Stage W/input impedance increased.	12